

# Reading Circuit Diagrams

Important concepts:

1. The battery is not drawn in a circuit diagram. Notice 6V and 0V - these are the positive and negative connections.

2. Rather than a complete circuit you now have to get used to a **TOP** and **BOTTOM RAIL**.

3. It is common practice to switch the positive or TOP rail.



